




MASSEY UNIVERSITY

Multiple-accumulator CMACs and FX correlator efficiency

Stepan Lapshev


Supervisor: Dr Rezaul Hasan

Original FX architecture

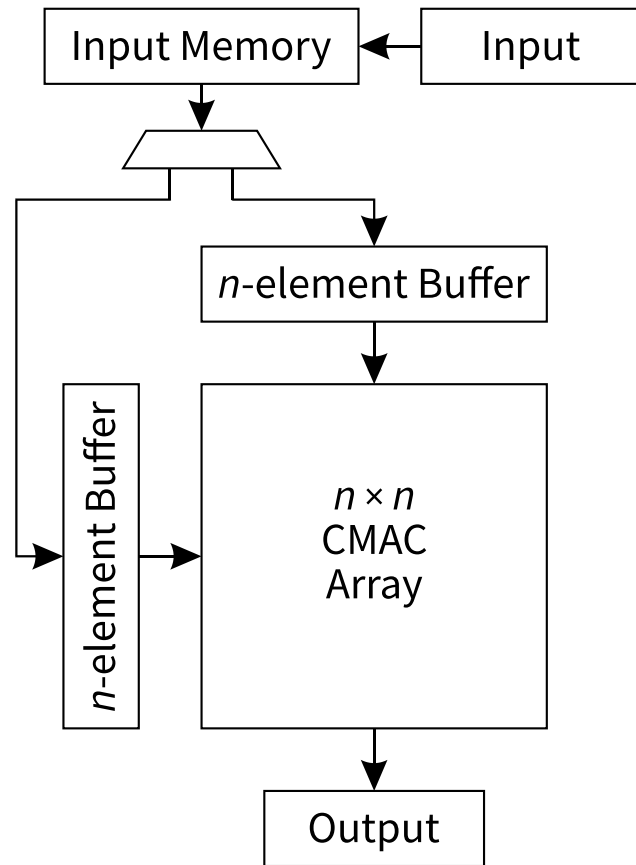

- The on-chip memory stores data samples for all $2N$ signals for a portion of frequency channels
- Input signals are split into w sets of n signals for CMAC processing
- Two sets of n signals are correlated with each CMAC operation
- One accumulation produced by the CMAC array is called a sub-integration (SI)

Pattern of SIs

 

Architecture pros/cons

Advantages:


- Every sample is delivered to only one processing chip
- Flexible with respect to N and the bandwidth
- Scales easily
- Can be made using standard technologies


Disadvantages:

- Every data sample is read w times from the memory because it is used in w SIs
- Often a memory-limited design: 2 memory operations per 1 CMAC operation


Improvement: Multiple-accumulator CMACs

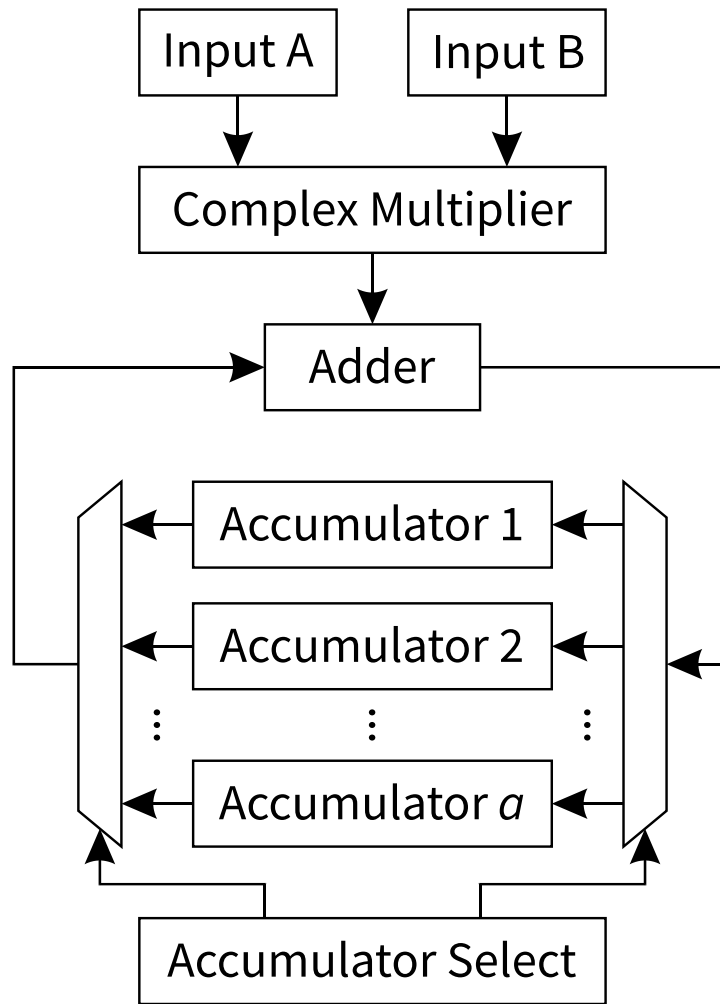- Use CMACs with $a > 1$ accumulators
- Group SIs that share input signals into groups of a
- When processed in correct sequence, this allows to reuse data samples currently in the processing buffer
- This significantly reduces the number of memory operations for the same number of CMAC operations, the same input and the same output



 

$w = 5, a = 1$

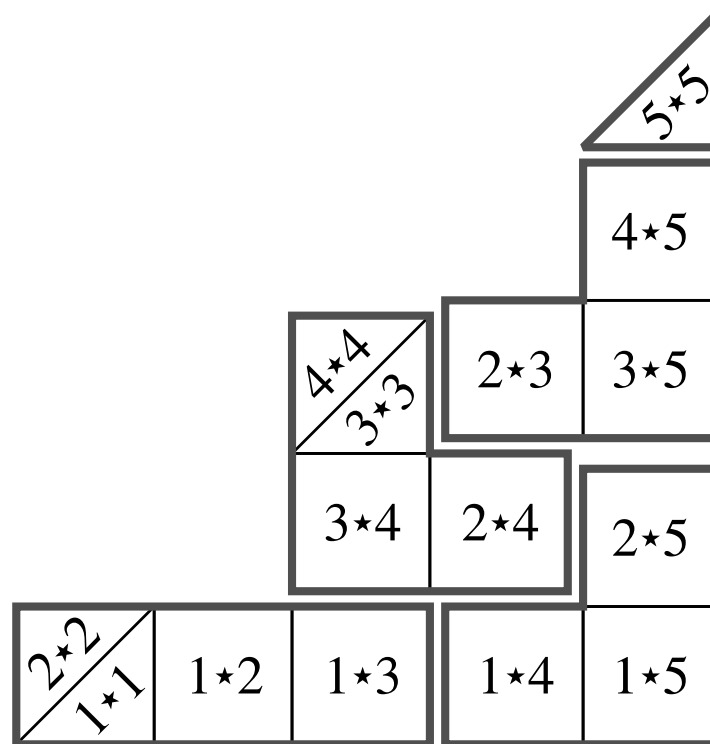

$w = 5, a = 3$

Reduction in memory quantified: Number of read operations R

$$R(a, w) = (a + 1) A + (B + 1) \operatorname{sgn} B - \left\lfloor \frac{w}{2} \right\rfloor \operatorname{sgn} (a - 1) \\ + (w \bmod 2) (1 - \operatorname{sgn} B),$$

where

$$A = \left\lfloor \frac{\lfloor w^2/2 \rfloor}{a} \right\rfloor$$

and


$$B = \left\lfloor \frac{w^2}{2} \right\rfloor \bmod a.$$

Reduction in memory quantified:
Improvement ratio /

$$I(a, w) = \frac{R(a, w) + w}{w^2 + w}$$

$$I \simeq \frac{a + 1}{2a}$$


Reduction in memory quantified

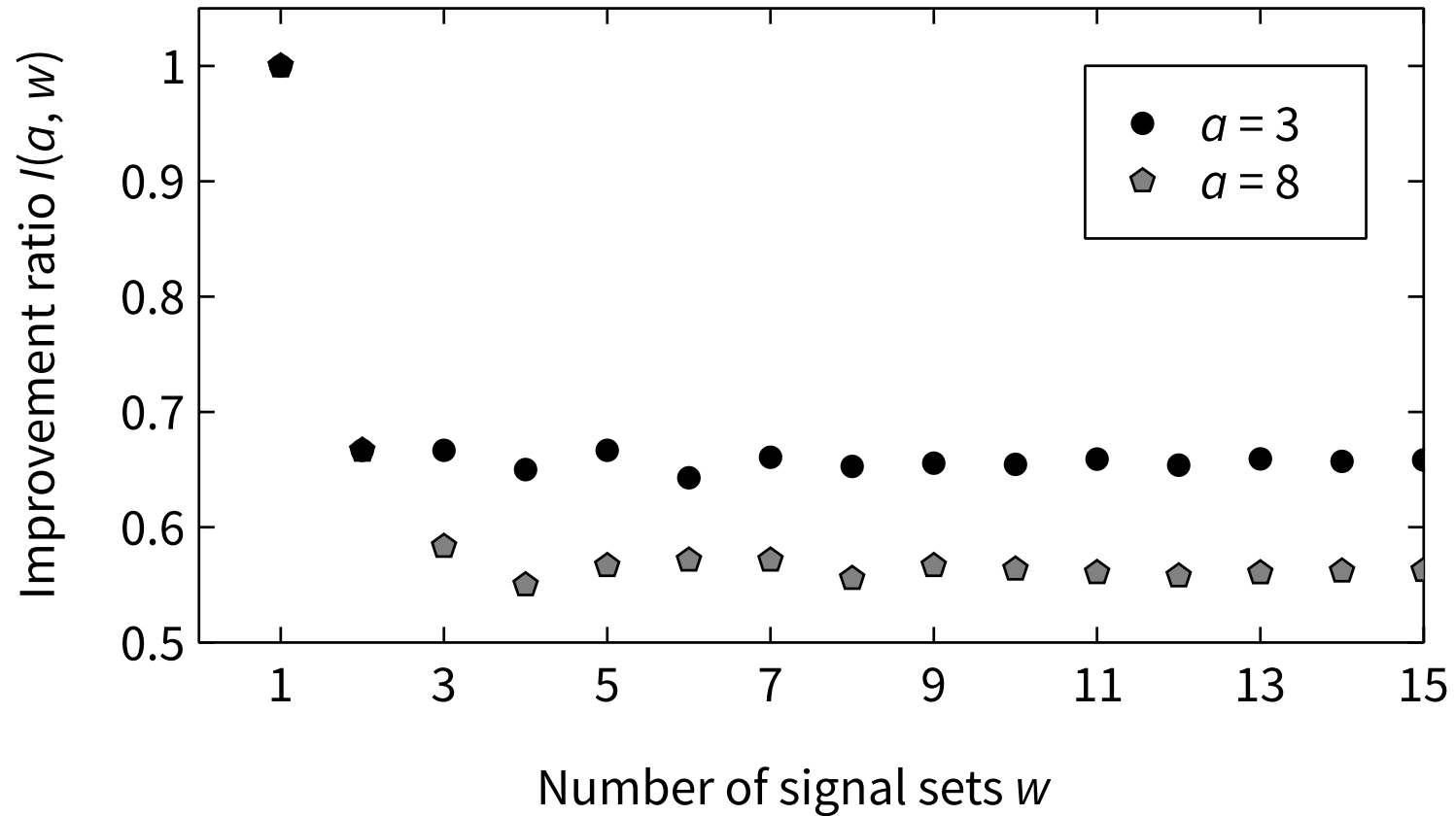


Hardware implementation

- Implementation of 8-bit CMACs in a high-performance 28 nm CMOS process
- Custom design of equivalent $a = 1$ and $a = 3$ designs to evaluate advantage of the multiple-accumulator approach
- Important to find out that memory savings are not overwhelmed by any increase elsewhere

Accumulator storage cell design

 


$a=1$

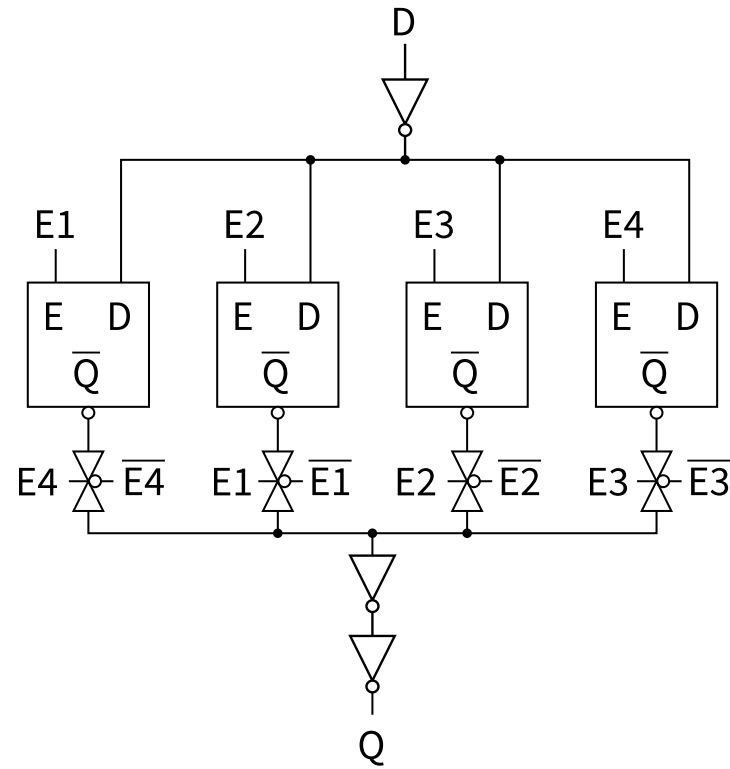








$a=3$

CMAC design








Correlation: $(a + ib)(c - id)$

 

      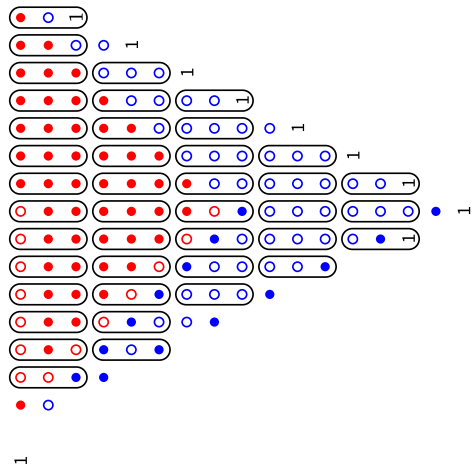
- Two-stage pipeline: multiplication and accumulation
- Fused multiplier design based on logarithmic reduction adder trees: highest efficiency in terms of energy per operation and circuit delay
- Soft-edge flip-flops between stages to increase timing performance





Im

       


Re

 

 

 

 

Simulation results

Parameter or Metric	Value	
Temperature, °C	60	
Cycle time, ns	0.8	
Accumulator count a	1	3
Total energy/op, pJ	2.614	2.578
Multiplier energy/op, pJ	1.619	1.373
Accumulator energy/op, pJ	0.995	1.205
Total leakage, μA	228.8	243.1
Accumulator leakage, μA	60.3	74.6
Circuit area, μm^2	3950.2	4160.6